

# Syllabus

18 June 2024 14:27



EEEE-syllab  
us

Course Code	Name of the Course				
216U06C106	<b>EEE</b> Elements of Electrical and Electronics Engineering				
Teaching Scheme (Hrs./Week)	TH	P	TUT	Total	
	03	--	--	03	
Credits Assigned	03	--	--	03	
Evaluation Scheme	Marks				
	LAB/TUT CA	CA (TH)		ESE	
		IA	ISE		
	--	20	30	50	100
<b>Course pre-requisites:</b> Knowledge of Basic Electrical parameters: Resistance, Inductance, Capacitance, Frequency, Voltage, Current and Power and Energy, basic laws of magnetism					<i>IA<sub>1</sub>, IA<sub>2</sub> → 50</i>
<b>Course Objectives:</b> It is difficult to imagine life without electricity and electronics. Electricity plays a major role in the working of all minor and major devices used in our day to day life. In this course students acquire fundamental knowledge to understand the design of electrical and electronics systems.					
<b>Course Outcomes (CO):</b> <ul style="list-style-type: none"> <li>CO1. Analyse resistive networks excited by DC sources using various network theorems</li> <li>CO2. Demonstrate and analyse steady state response of single phase and three phase circuits</li> <li>CO3. Understand principles and working of AC and DC machines with their applications.</li> <li>CO4. Explain rectifier-filter circuits using PN junction diode and voltage regulator circuits using Zener diode</li> <li>CO5. Understand Bipolar Junction transistor and its applications</li> </ul>					

Module No.	Unit No.	Contents	No of Hrs.	CO			
1	DC circuits	1.1 Concept of dependent and independent sources, ideal and practical voltage and current sources, Kirchhoff's Laws, source transformation and network terminology. 1.2 Resistive network simplification, Series, parallel connection and Star-Delta transformations 1.3 Mesh and nodal analysis, concept of super mesh and super node (Analysis only with independent sources) 1.4 Superposition theorem, Thevenin's theorem, Norton's theorem, Maximum power transfer theorem (Analysis only with independent sources)	12	CO1			
<i>100% Concept</i>							
<i>90% Numericals</i>							
<i>10% Theory</i>							
2	AC circuits	2.1 Generation of alternating voltage, average value, RMS value, form factor, crest factor, phasor representation in rectangular and polar form. 2.2 Steady state behaviour of single phase AC circuits with pure R, L, and C, concept of inductive and capacitive reactance, phasor diagram of impedance, phase relationship in voltage and current. 2.3 RL, RC and RLC series and parallel circuits, concept of impedance and admittance, power triangle, power factor, active, reactive and apparent power, concept of power factor improvement. 2.4 Series and parallel resonance, Q-factor and bandwidth 2.5 Three-phase balanced circuits, voltage and current relations in star and delta connections. 2.6 Measurement of power in 3-phase system using two wattmeter method	15	CO2			
<i>100% concept</i>							
<i>80% Numericals</i>							
<i>10% Th.</i>							
3	Electrical Machines	3.1 Single phase transformer construction and principle of working, emf equation of a transformer, losses in transformer, equivalent circuit of Ideal and practical transformer, voltage regulation and efficiency of transformer, phasor diagram at various loading condition (No numerical expected) 3.2 Construction and working principle of DC motors such as series, shunt and compound, torque-speed characteristics, selection criteria and applications (no derivations and numerical expected) 3.3 Single phase induction motor: Construction, working principle, double field revolving theory, split phase, capacitor start and shaded pole motor. applications (no derivations and numerical expected) 3.4 Three phase induction motor: Construction, working principle, Generation of rotating magnetic field, applications. (no derivations and numerical expected)	12	CO3			
<i>100% Theory</i>							
<i>10% Numericals</i>							
<i>10% Th.</i>							
4	Diodes and their applications	4.1 P-N Junction diode: Construction and working of PN junction diode, current voltage characteristics. Application as Rectifier: Half wave rectifiers with resistive load,	04	CO4			
<i>100% Concept</i>							
<i>90% Numericals</i>			<i>10% Th.</i>				



		full wave center tap and bridge rectifier with resistive load with their parameters such as ripple factor, rectification efficiency, transformer utilization factor. Filter circuits		
	4.2	<b>Zener Diode:</b> Construction and working, current voltage characteristics. <b>Application of Zener diode:</b> Voltage regulator		
	4.3	<b>Light emitting diode (LED) and Photo Diode:</b> Construction and working, current voltage characteristics and applications		
<b>5</b>	<b>Bipolar Junction Transistor and their applications</b>			03 CO5
<b>100% Theory</b>	5.1	<b>Bipolar Junction Transistor (BJT):</b> BJT construction and operation, Common-Base (CB), Common-Emitter (CE) and Common-Collector (CC) configurations and input and output characteristics, operating point, DC biasing (No Numerical expected)		
	5.2	Application of BJT-CE configuration: Voltage amplifier, Electronic Switch (No Numerical expected)		
<b>Self-learning topics#</b>			--	--
		Components of LT Switchgear: Switch Fuse Unit (SFU), MCB, ELCB, MCCB Types of Wires and Cables, Earthing Types of Batteries, Important Characteristics for Batteries, Elementary calculations for energy consumption, power factor improvement and battery backup Lamps- fluorescent, CFL, LED Electrical measuring instruments principle and applications- energy meter, megger, tong tester.		
<b>Total</b>			<b>45</b>	<b>--</b>

# Students should prepare all self-learning topics on their own. Self-learning topics will enable students to gain extended knowledge of the topic. Assessment of these topics may be included in IA.

### References

Sr. No	Name/s of Author/s	Title of Book	Publisher	Edition/ Year
1	B. L. Thereja	Electrical Technology Vol-I and Vol-II	S. Chand	25 <sup>th</sup> Edition 2014
2	Mittle and Mittle	Basic Electrical Engineering	Tata McGraw Hill, India	2 <sup>nd</sup> edition (New) 2001
3	Singh Ravish R.	Basic Electrical Engineering	S. Chand	1 <sup>st</sup> Edition, 2023
4	B.R. Patil	Basic Electrical Engineering	Oxford University Press	2 <sup>nd</sup> Edition, 2022
5	Donald Neamen	Microelectronics: Circuit Analysis and Design	Tata McGraw Hill India	4 <sup>th</sup> Edition 2021

IA

18 June 2024 14:30

Voltage → unit → V → Potential difference between any two points in electric N/w.

$$1V = \frac{1J}{1C} = \frac{1 \text{ J of energy (workdone)}}{\text{unit charge}}$$

Electric charge → Value of electrons  
 $\hookrightarrow 1.062 \times 10^{-19} C$


2) Electric current → unit → Amp → I

Rate of flow of electrons in Conductor.  
 or  
 Semiconductor

$$1A = \frac{1C}{1\text{ sec}}$$

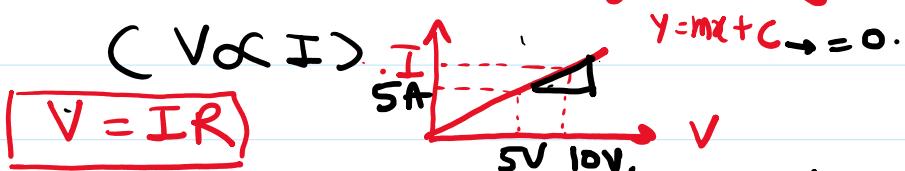3) Ohms law

Potential difference between any two points on a conductor is directly proportional to current flowing through it.



(Provided materials length, cross-section area is const).

Where R is the resistance between

two points

Limitations of Ohms law:-

1) Not applicable to non metallic conductor.

I

1) Not applicable to non metallic conductor.

2) Not applicable for nonlinear devices. (BJT, MOSFET, diode)

3)

Resistance  $R \rightarrow$  

$$R = 10\Omega$$

$$10K \rightarrow 10 \times 10^3$$

It is the property of a material due to which it opposes current flowing through it.

e.g. conductors

↳ opposes very low resistance

Insulators

↳ opposes very high resistance

$$R \propto L_{\text{conductor}}$$



$$\propto \frac{1}{A} \quad A \rightarrow \text{area of cross-section of conductor}$$

depends on nature of conductor

↳ on temperature of conductor

$$R = \rho \frac{L}{A}$$

$\rho_{\text{HO}}$

$\rho \rightarrow$  Resistivity of material.

PTC      NTC  
 $T \uparrow R \uparrow$      $T \uparrow R \downarrow$

# Electric Power (P)  $\rightarrow$  (DC)  
(W)  $\rightarrow$  unit

$$P = V \cdot I - ①$$

$$= I^2 R - ②$$

$$= I^2 R - \textcircled{2}$$

$$= \frac{V^2}{R} - \textcircled{3}$$

## # Types of sources

↳ Supplies energy  
to electric N/W



### Sources



✗ Dependent

V<sub>CVS</sub>  
CCCS  
VC<sub>CS</sub>  
CC<sub>V</sub>S

✓ Independent


O/P of sources  
is not dependent  
on any n/w  
Variable  
(time varying)

### Ac & Dc Sources

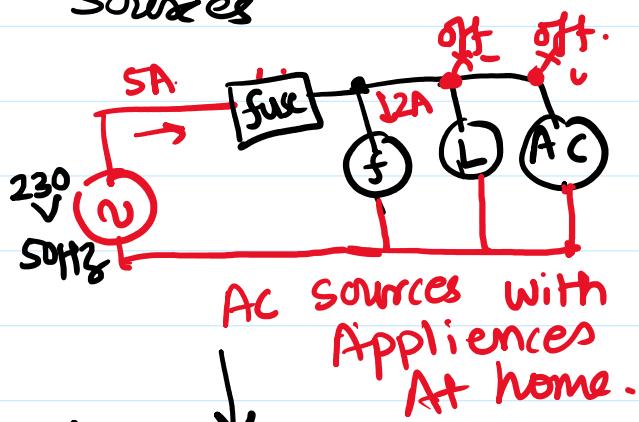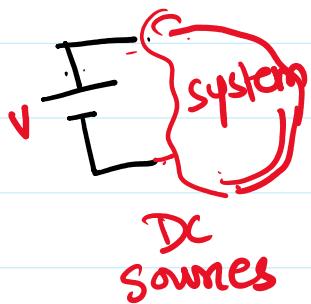


$\frac{1}{T_{\text{sec}}}$



$f = 50 \text{ Hz}$

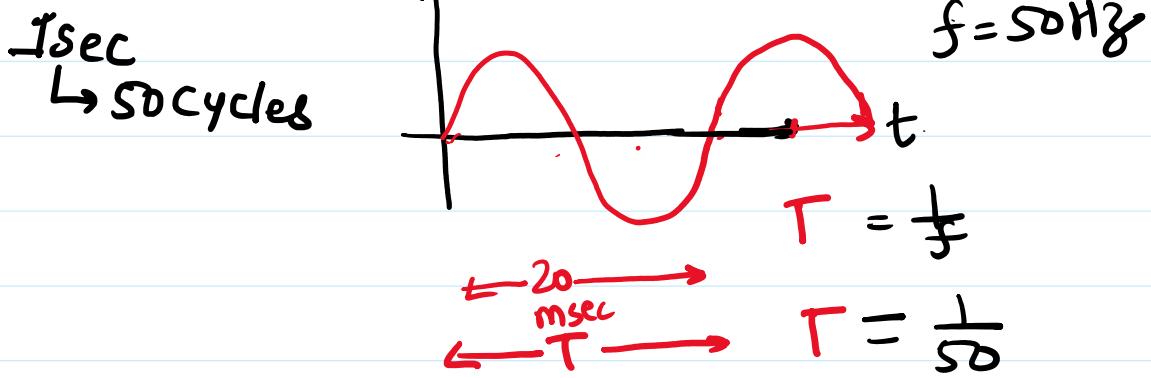

# Independent voltage source.

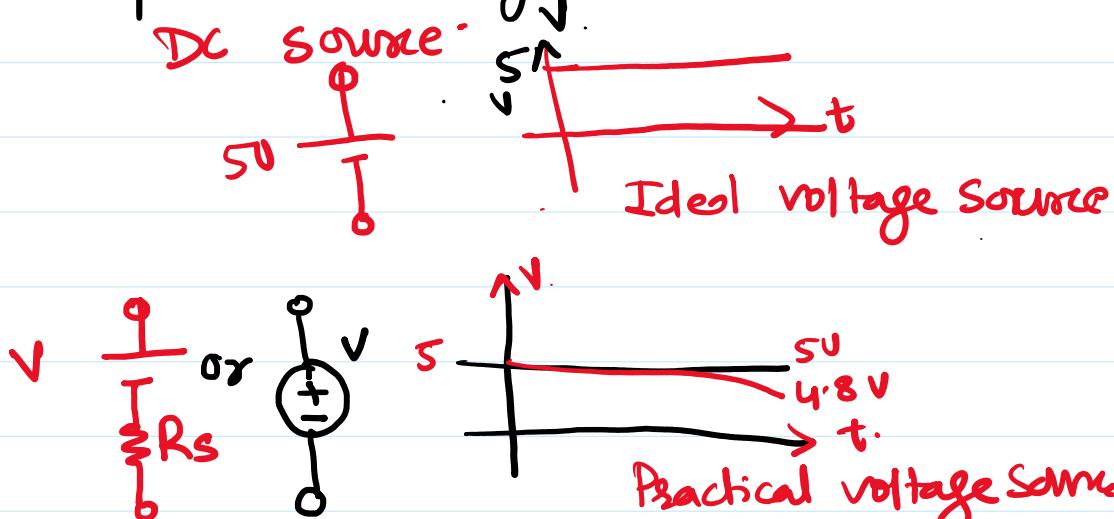

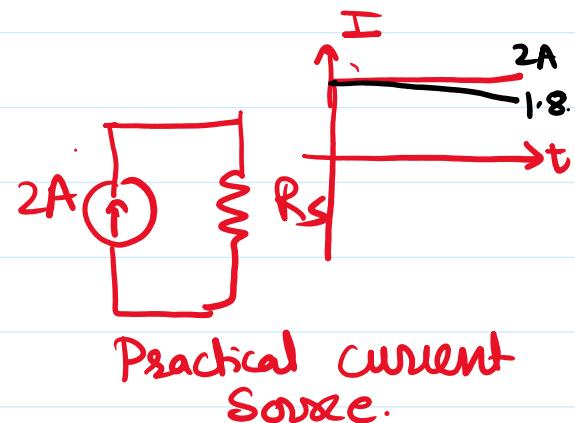
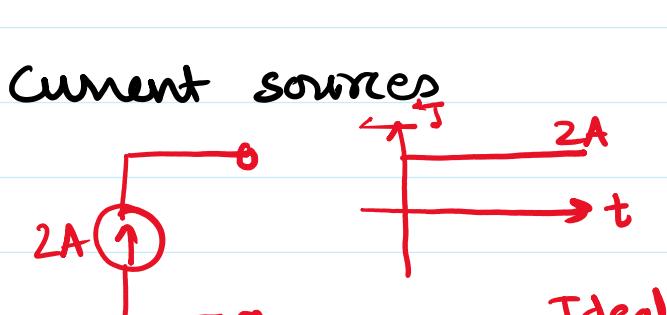
$f = 0$   
(due to voltage drop)  
as current flows.




Summary till now  
→ Voltage, Current, Power, Sources

# Source transformation.



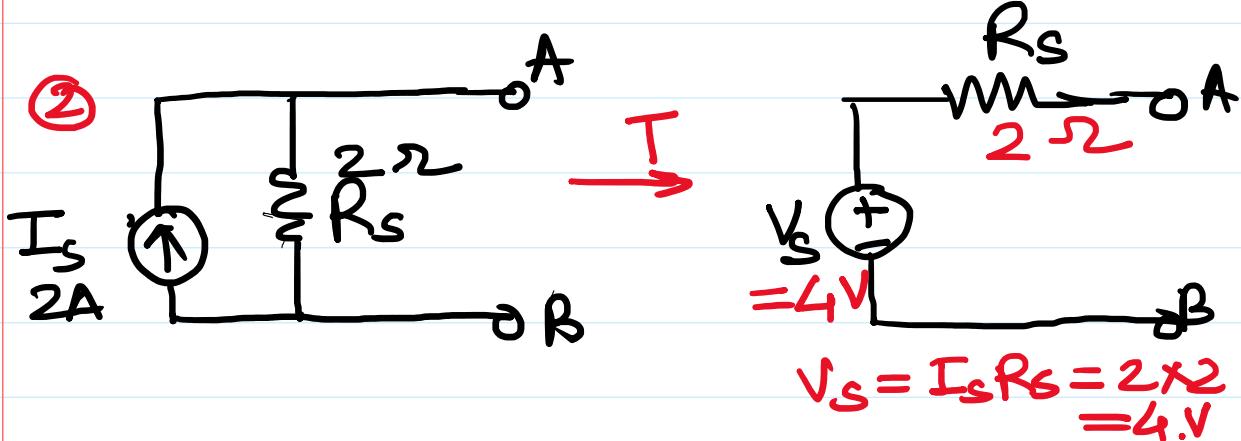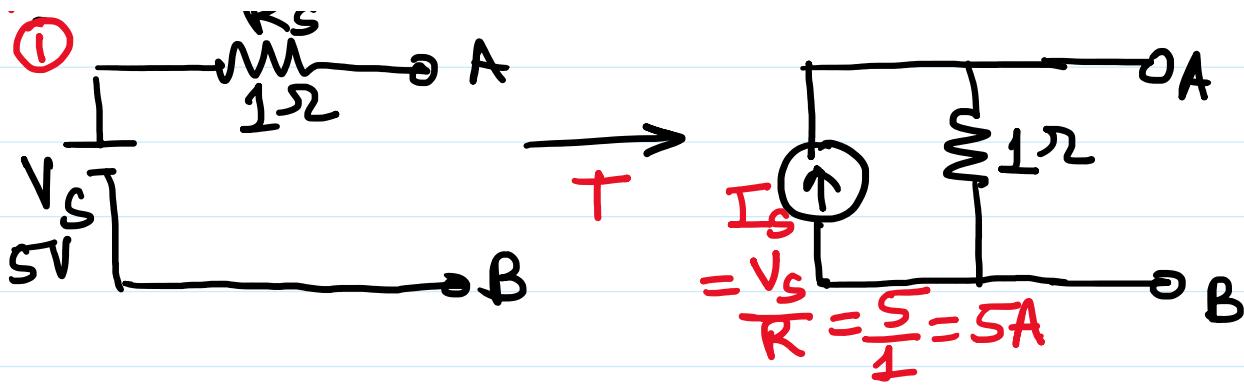

## # Resistive Network simplification

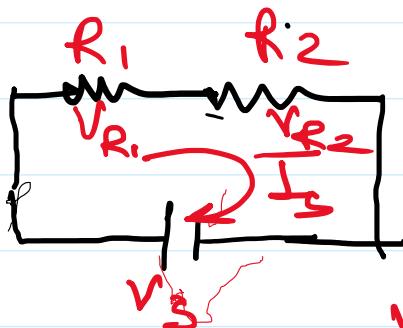

$$V_s = V_{R_1} + V_{R_2} = I_s R$$

$$V_{R_1} = I_s R_1$$

$$V_{R_2} = I_s R_2$$

$$V_s = I_s R_1 + I_s R_2 = I_s (R_1 + R_2)$$

$$V_s = \overline{I_s} \overline{R_T}$$

Observations

→ Same current flows through both  $R$

$\therefore R \rightarrow$  in series  $\rightarrow V \rightarrow$  additive




$$R_T = 6 + 4 + 2 = 12 \Omega$$


$$I_s = \frac{V_s}{R_1 + R_2} \quad \text{--- (1)}$$

$$V_{R_1} = I_s R_1 = \left( \frac{V_s}{R_1 + R_2} \right) R_1 \quad \begin{array}{l} \text{Voltage} \\ \text{division} \\ \text{Rule} \end{array}$$

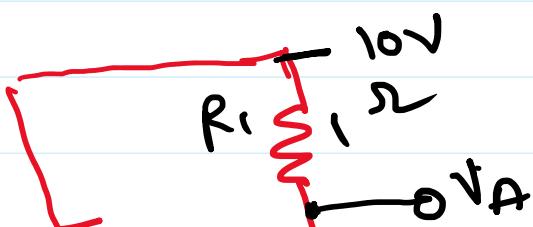
$$V_{R_2} = I_s R_2 = \left( \frac{V_s}{R_1 + R_2} \right) R_2$$


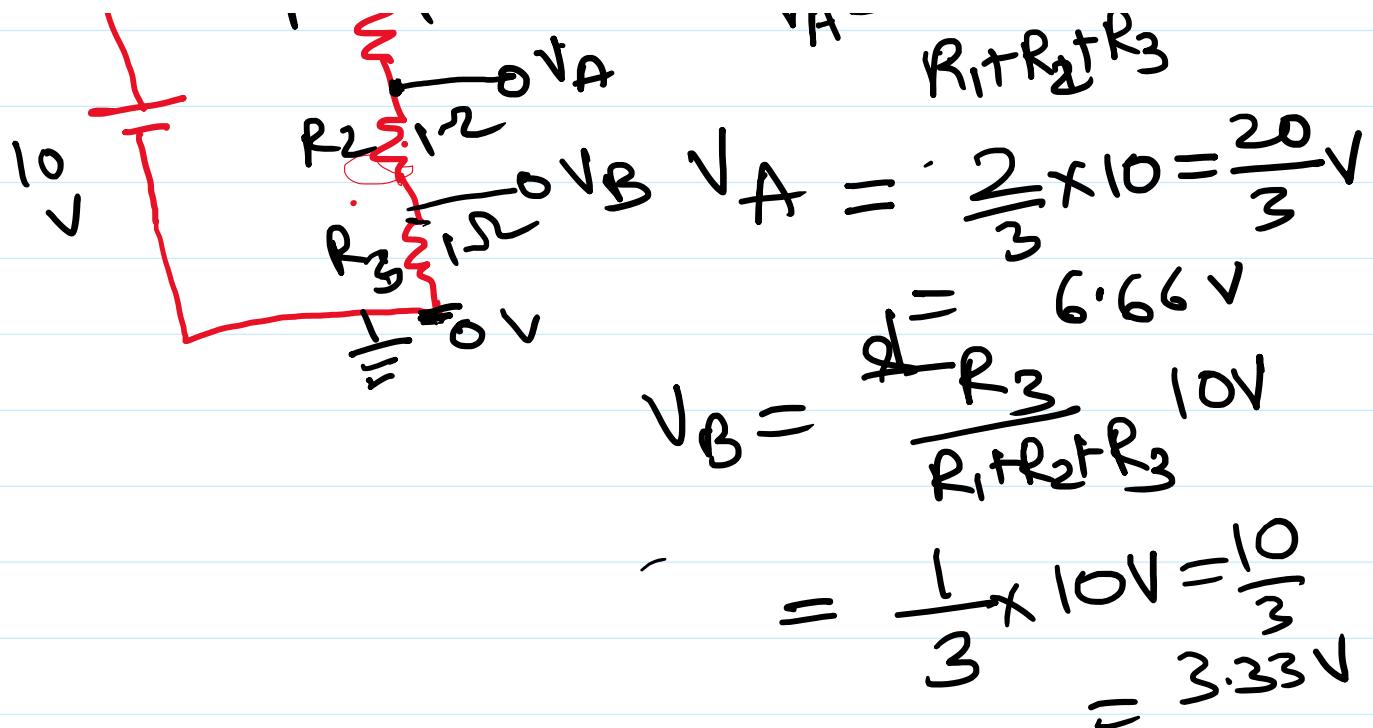
$$V_A = \frac{R_2 + R_3}{R_1 + R_2 + R_3} 10V$$



# Parallel circuit

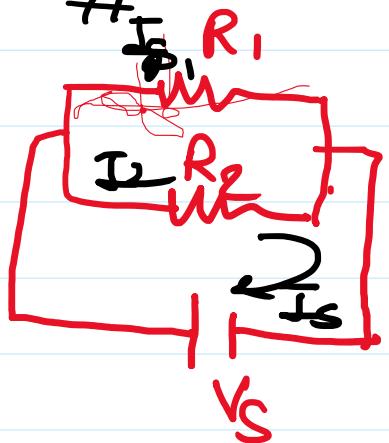

$$V_s = I_1 R_1 + I_2 R_2$$

$$V_s = I_s R_t$$

$$V_s = I_s (R_1 || R_2)$$

$$V_s = I_s \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$V_s = I_1 R_1 = I_2 R_2$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

~~$$\frac{1}{R_t} = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$~~

$$\frac{R_1 || R_2 }{\frac{R_1 R_2}{R_1 + R_2}} || R_3$$

$$\frac{R_1 R_2}{R_1 + R_2} || R_3$$

$$\frac{\frac{R_1 R_2}{R_1 + R_2}}{10 \parallel 10 \parallel 10} \rightarrow \underline{\underline{10 \parallel 10 \parallel 10}}$$

$$\frac{100}{20} \parallel 10$$

$$\underline{\underline{5 \parallel 10}}$$

$$\frac{50}{15} = 3.05 \Omega$$

# Current division Rule


$$V_s = I_1 R_1 = I_2 R_2$$

$$I_1 = \frac{V_s}{R_1} = , \quad \left( \frac{1}{R_1} \times \frac{R_1 R_2}{R_1 + R_2} \right) I_s$$

$$I_1 = \left[ \frac{I_s}{R_1 + R_2} \right] R_1 \quad \begin{matrix} C \\ D \end{matrix}$$

$$I_2 = \left[ \frac{I_s}{R_1 + R_2} \right] R_2 \quad R$$

Numerical 1

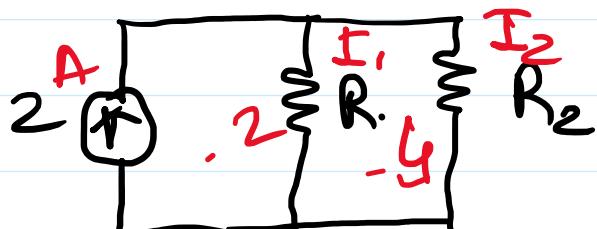


$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) 2 = \frac{1}{2} \times 2^A$$

$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) 2 = \frac{1}{2} \times 2^A = 1^A$$


$$I_1 = \frac{4}{3} A, I_2 = \frac{2}{3} A$$

# Open Ckt & Short Ckt.

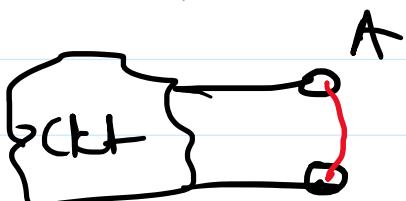

$$R_{AB} = 0 \quad V_{AB} = 0 \quad S_C$$


$$I_{AB} = \infty$$

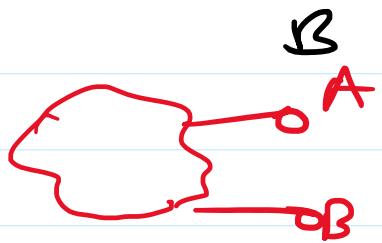

$$R_{AB} = \infty$$

$$V_{AB} \neq 0$$

$$I_{AB} = 0$$


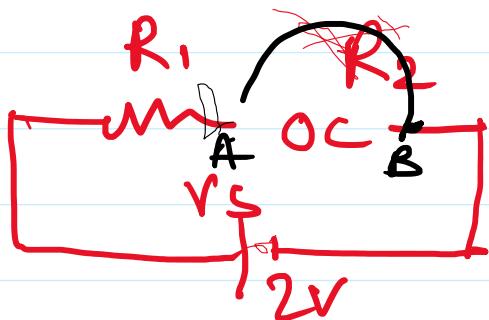


$$V_{AB} =$$

$$I_S = \frac{V_S}{R_1 + R_2}$$

$$R_{AB} =$$

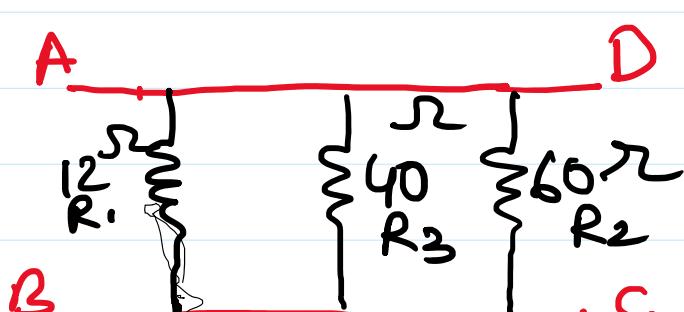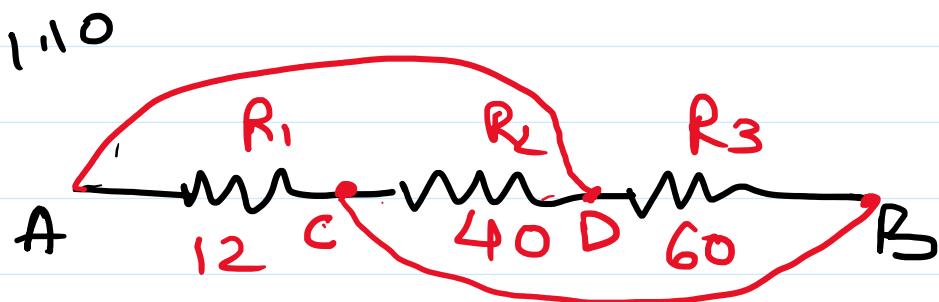Numerical  $\rightarrow$  find equivalent Resistance between A & B.






$$R_1 \parallel R_2 \parallel R_3$$

$$\frac{12 \parallel 40 \parallel 60}{480 \parallel 60}$$


$$= 8 \Omega$$

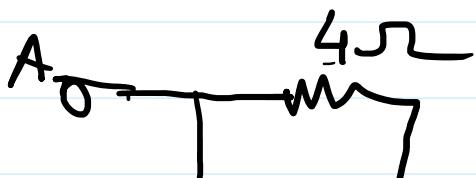1.11  $\rightarrow$  What is equivalent Resist in A & B



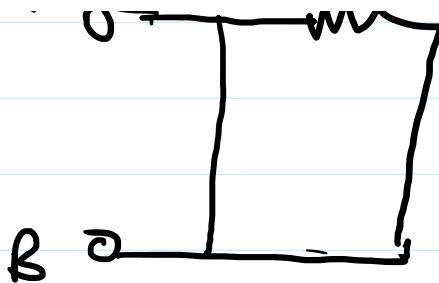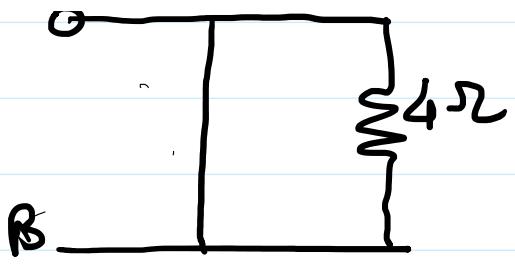

# Numerical 4 → find  $R_{AB}$

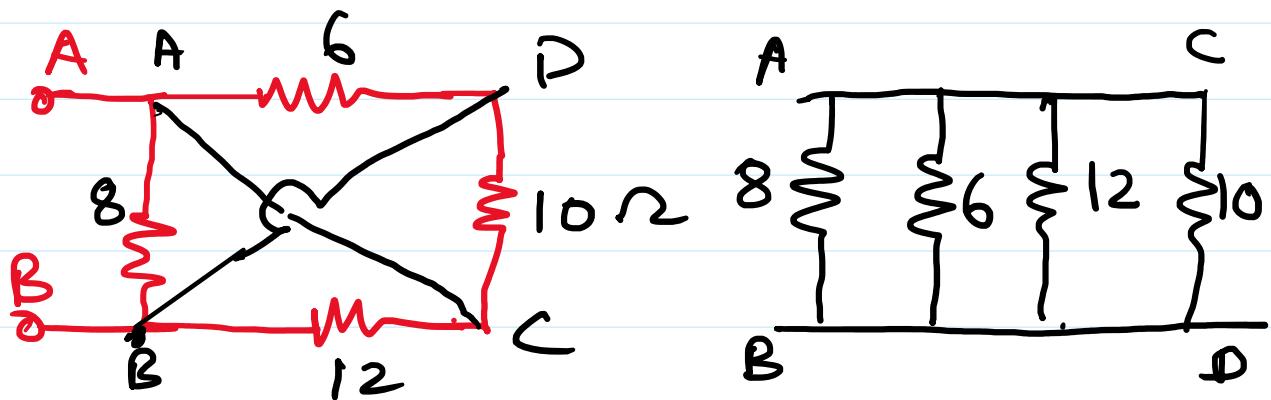

$$\frac{1}{R_T} = \frac{1}{8} + \frac{1}{6} + \frac{1}{12} + \frac{1}{10}$$


$$\frac{1}{R_T} = \frac{48}{14} + \frac{120}{22}$$


$$\frac{1}{R_T} = .$$

$$R_{AB} = \underline{8\ 1\ 6} \parallel \underline{1\ 2\ 1\ 1\ 0}$$

$$R_{AB} = 2.09 = 2.1 \Omega$$



Star to Delta transformation

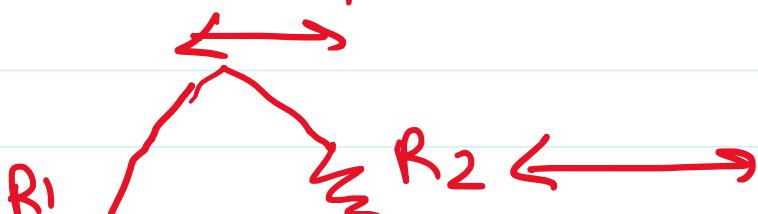

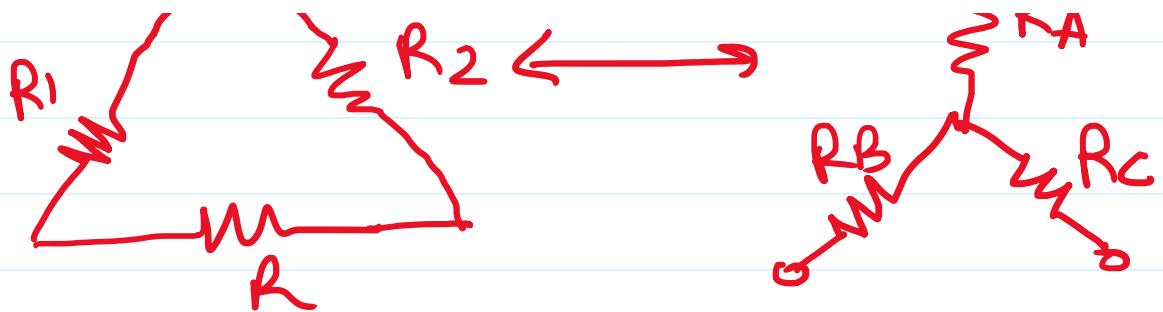

# Star to delta conversion



30 July 2024 10:50

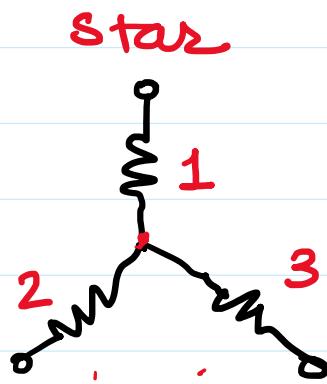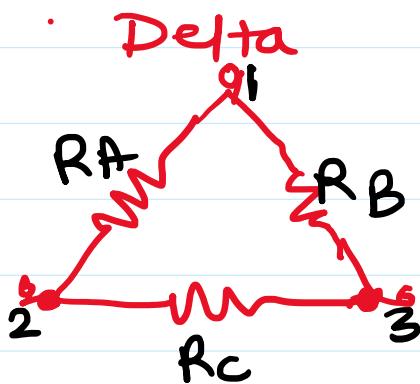

$$R_i = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A \cdot R_C}{R_A + R_B + R_C}$$

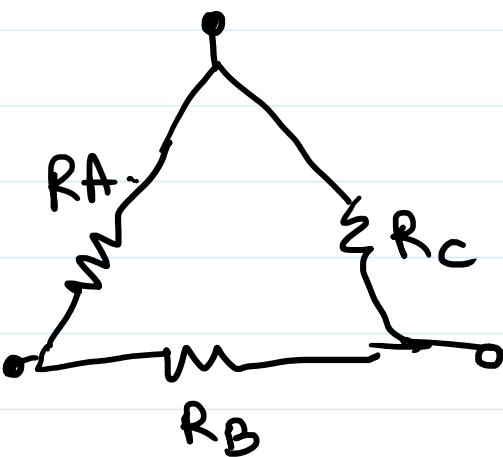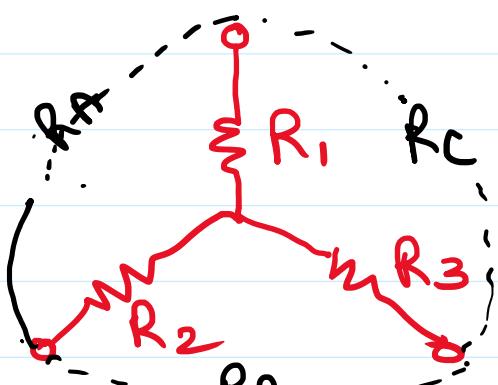
$$R_3 = \frac{R_B \cdot R_C}{R_A + R_B + R_C}$$



$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

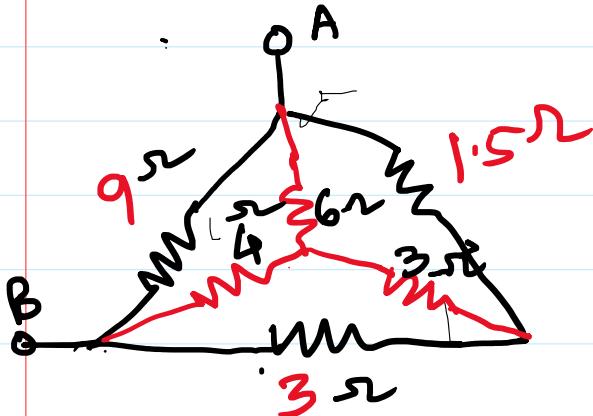Numerical 1 → find  $R_{AB}$ 

Always solve  
inner CKT  
first


find  $R_{AB}$

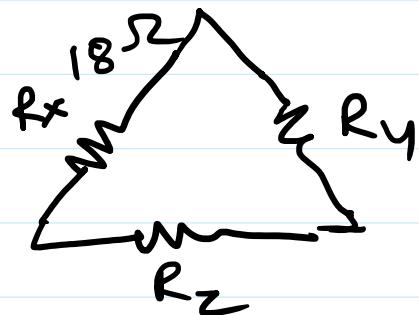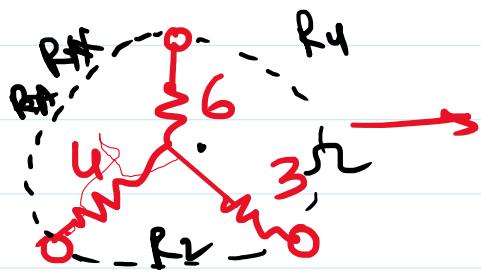

$$R_x = \frac{6 \times 4 + 6 \times 3 + 4 \times 3}{3} = \frac{24 + 18 + 12}{3} = 18 \Omega$$

$$R_y = \frac{54}{4} = 13.5 \Omega$$



$$R_z = \frac{54}{6} = 9 \Omega$$

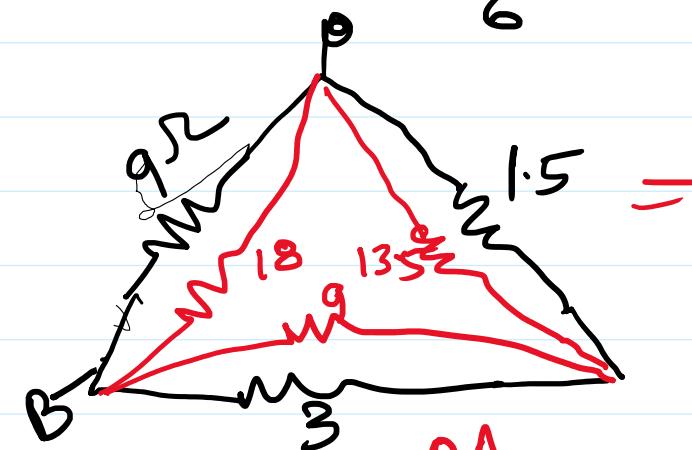


$$9 \parallel 18 = 6 \Omega$$




$$13.5 \parallel 1.5 = 1.3 \Omega$$

$$9 \parallel 1.3 = 2.25 \Omega$$

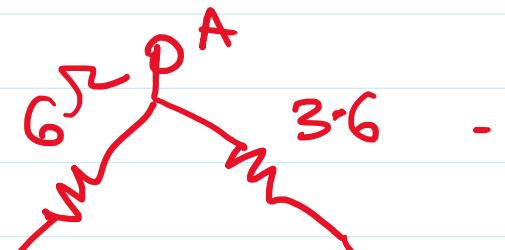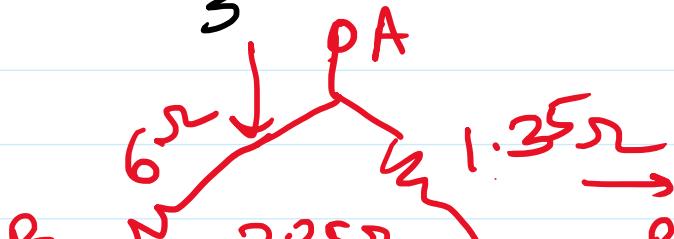

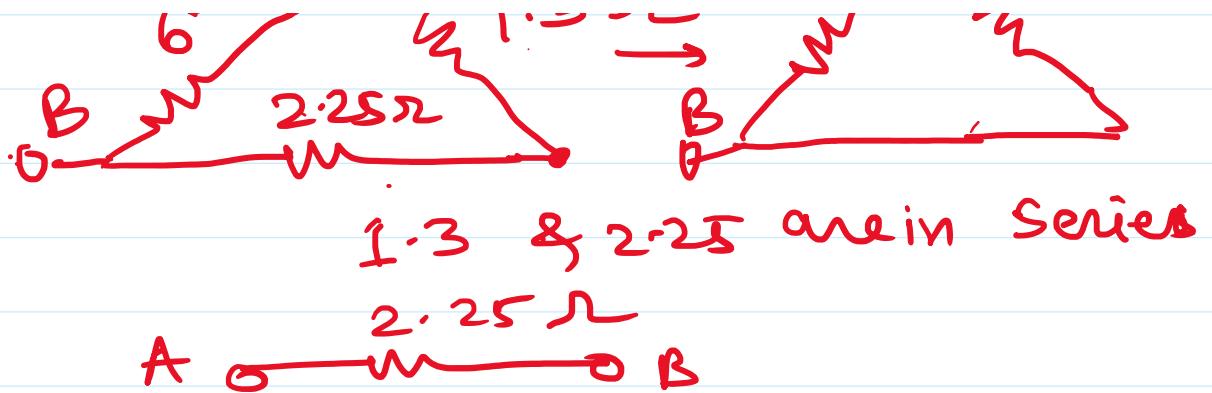


find  $R_{AB}$

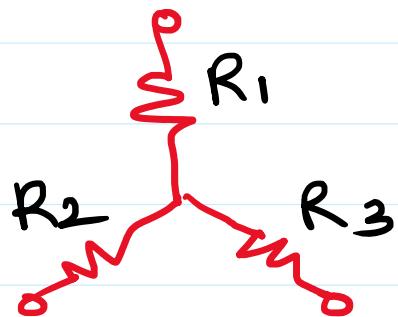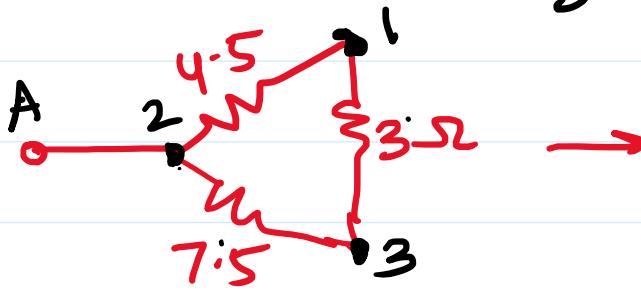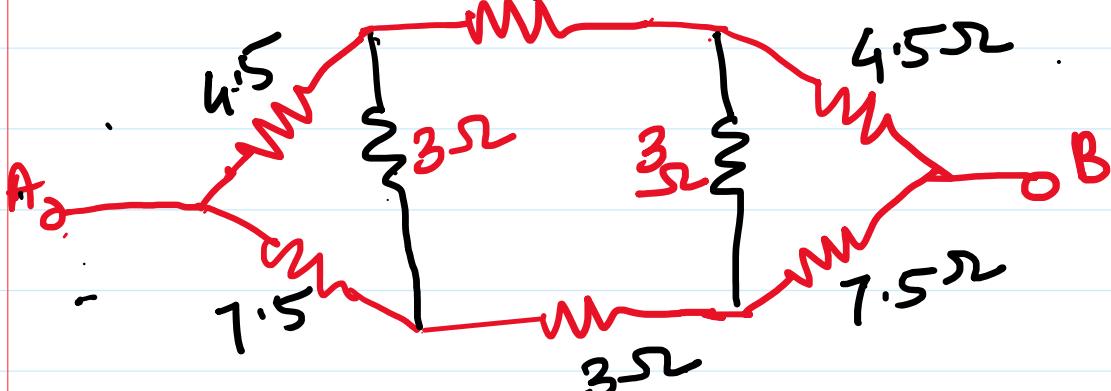

$$R_1 = \frac{4.5 \times 3}{4.5 + 7.5 + 3} = 0.9 \Omega$$


$$R_2 = \frac{4.5 \times 7.5}{15} = 2.25 \Omega$$
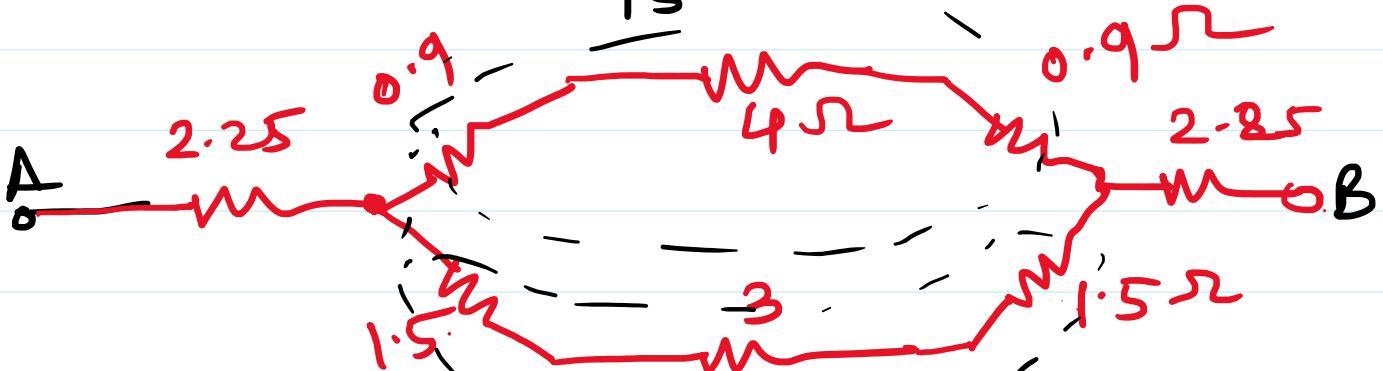
$$R_3 = \frac{7.5 \times 3}{15} = 1.5 \Omega$$







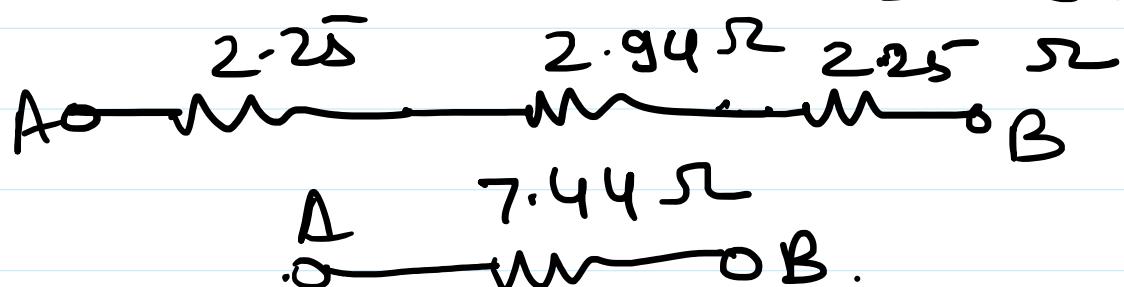
$$\text{Now } 5.8\Omega \parallel 6\Omega = \frac{5.8 \times 6}{5.8 + 6} = 2.94 \Omega$$




find  $R_{xy}$

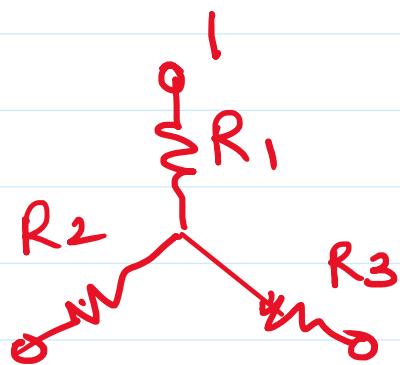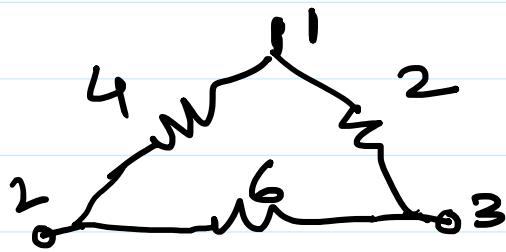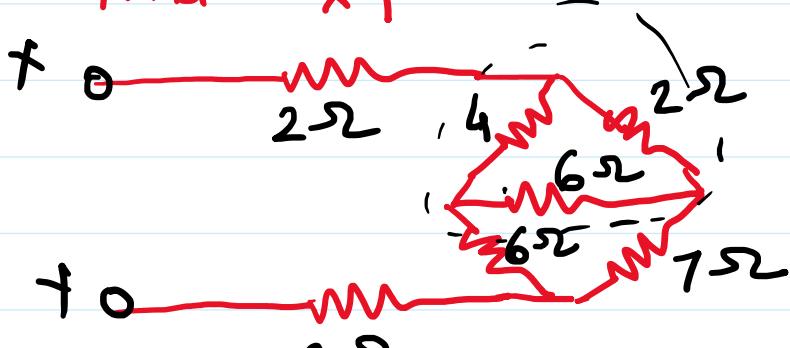


$$R_1 = \frac{4 \times 2}{6 + 4 + 2} = \frac{8}{12} = 0.67 \Omega$$


$$R_2 = \frac{6 \times 4}{ } = 2 \Omega$$
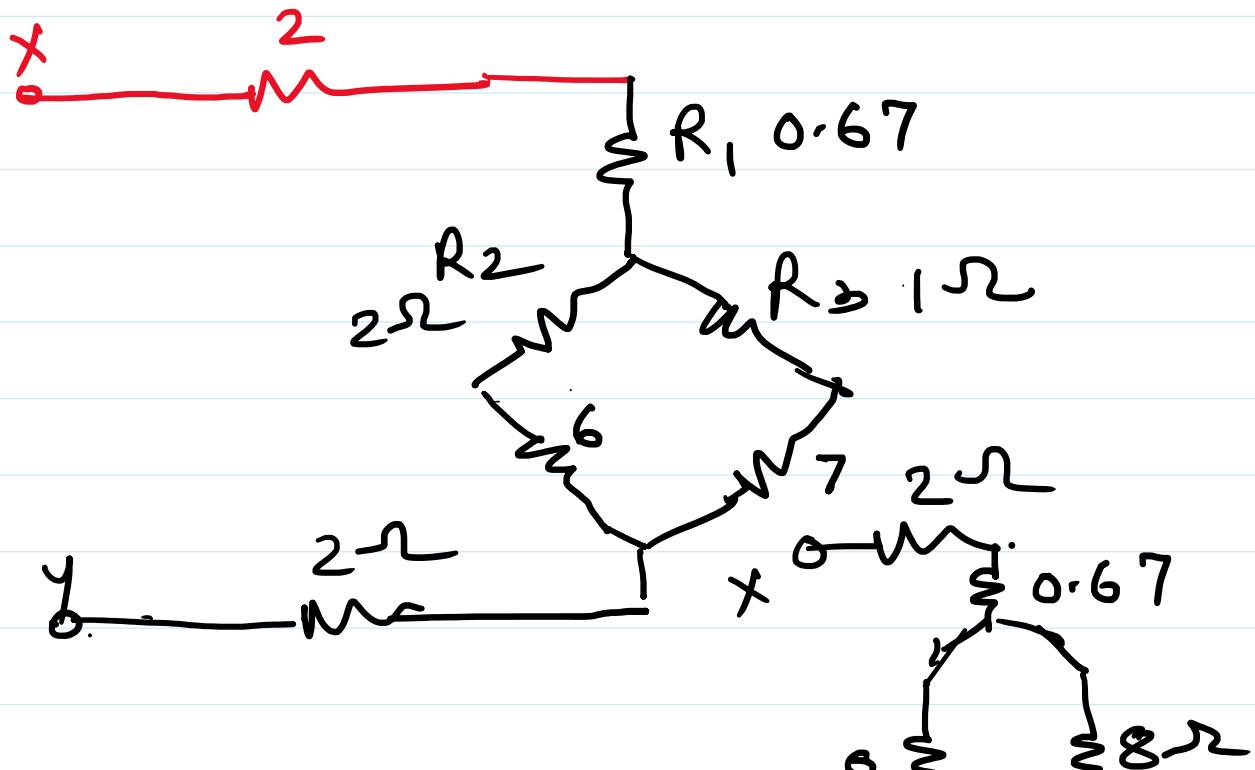
$$R_3 = \frac{12}{\frac{6+2}{12}} = 152$$




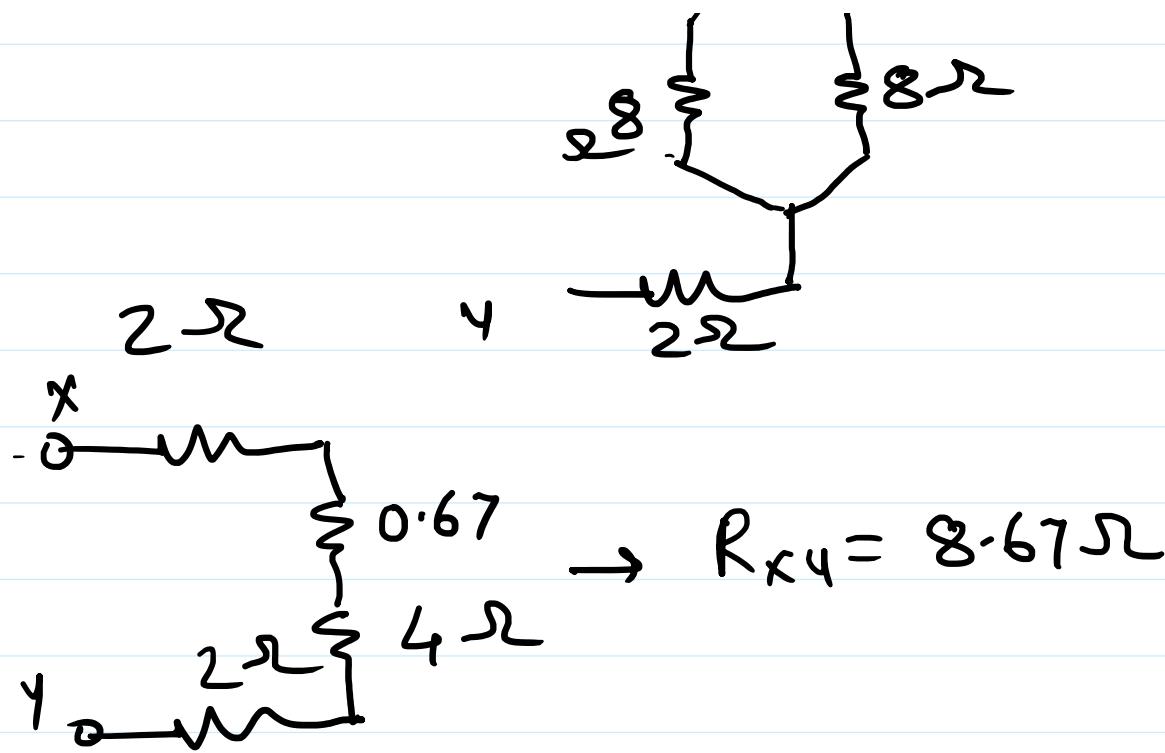

HW. find  $R_{xy}$

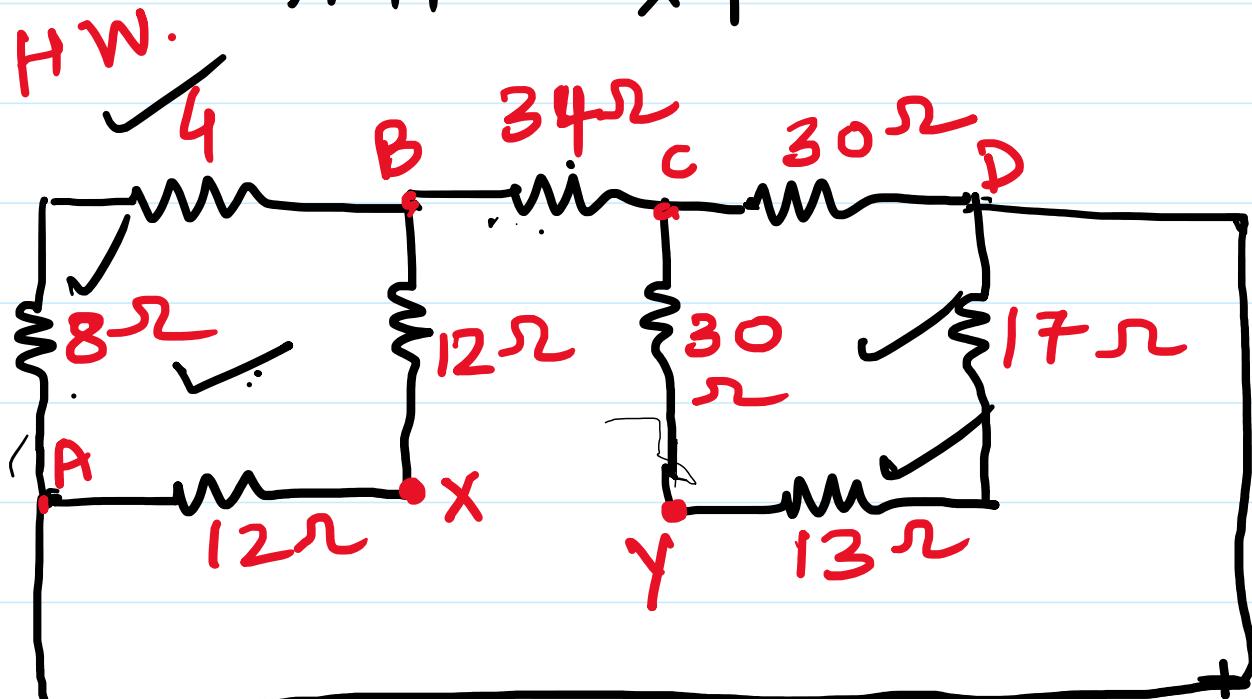

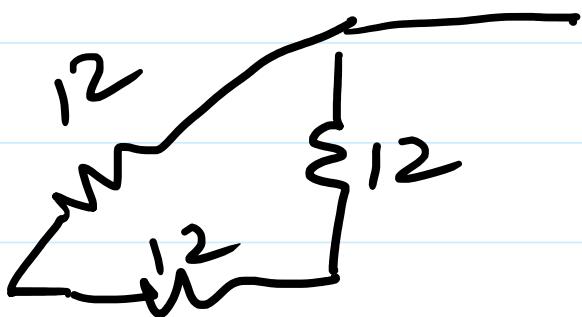Ans  $\rightarrow$   
 $R_{xy} = 24.84\Omega$



12 August 2024

18:52