

Course Name:	Elements of Electrical and Electronics Engineering Laboratory	Semester:	I/II
Date of Performance:	17 / 9 /2024	Batch No:	C5-2
Student Name:	Nidhesh Gamai	Roll No:	16014224025
Faculty Sign & Date:		Grade/Marks:	/ 20

Experiment No: 3

Title: Thevenin's Theorem & Norton's Theorem


Aim and Objective of the Experiment:

- To Verify for Thevenin's Theorem for the circuit
- To Verify Norton Theorem for the Circuit.



COs to be achieved:

CO1: Analyze resistive networks excited by DC sources using various network theorems.


Circuit Diagram:

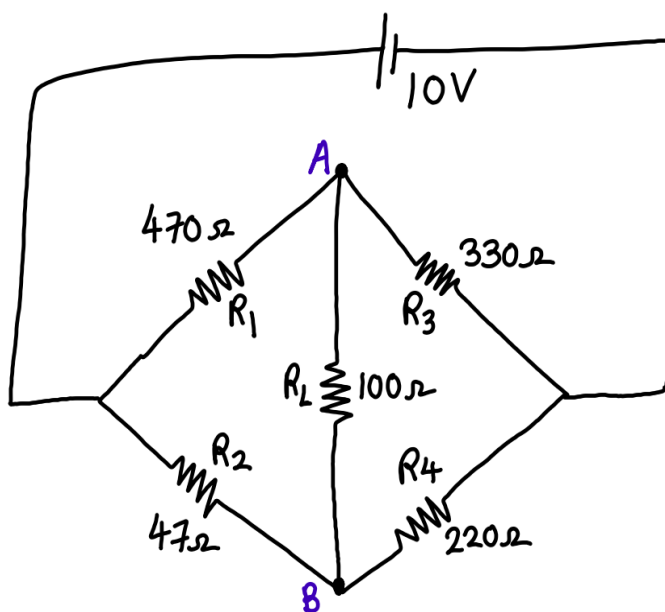


Task 1: Circuit Diagram to measure R_{TH}/R_N :

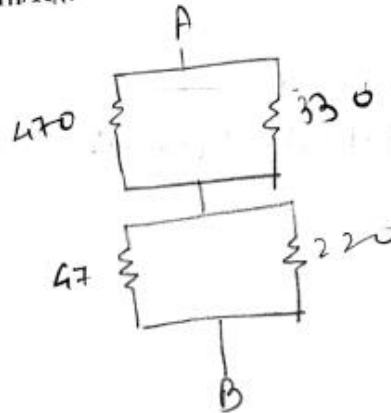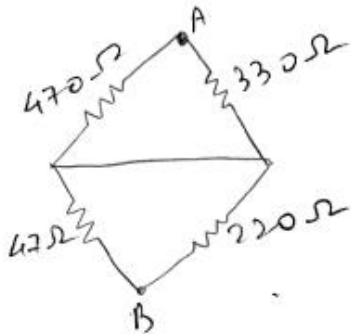

Task 2: Circuit Diagram to measure V_{TH} :

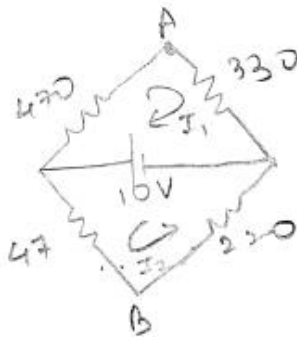

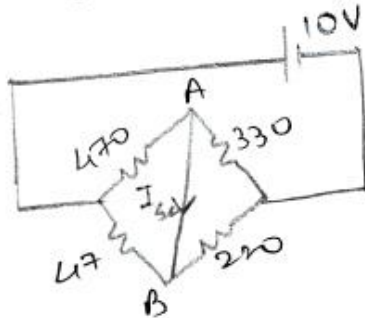Task 3: Circuit Diagram to measure I_{sc} :





Nidhesh Gama
CS-2 16014224025
[Signature]

Stepwise-Procedure:
Thevenin's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set 10V and measure open circuit voltage V_{Th} across load terminals A and B.
3. Replace all voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
4. Draw Thevenin's equivalent circuit and determine the value of load current from it.
5. Verify the results theoretically.

Norton's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set the voltages 10V
3. Remove the load resistance and measure the short circuit current I_{SC} through A and B terminals.
4. Replace all the voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
5. Draw Norton's equivalent circuit and determine the value of load current.
6. Verify the results theoretically

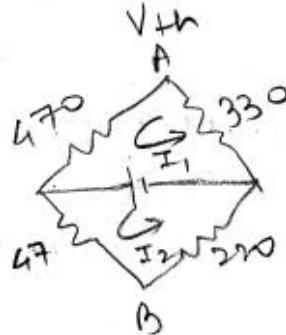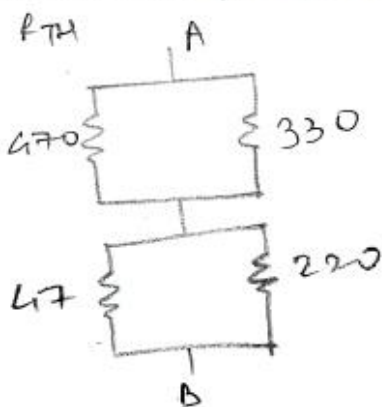Calculations: Thevenin's Theorem


$$V_B - 220I_2 - 330I_1 - V_A = 0$$

$$V_{AB} = -220I_2 - 330I_1$$

$$-10 - 470I_1 - 330I_1 = 0$$

$$I_1 = \frac{-10}{800} = -0.0125A$$

$$10 - 47I_2 - 220I_2 = 0$$

$$I_2 = \frac{10}{267}$$

$$I_2 = 0.0374A$$

$$R_{Th} = (470 \parallel 330) + (47 \parallel 220)$$

$$= \frac{470 \times 330}{470 + 330} + \frac{47 \times 220}{47 + 220}$$

$$= 232.60 \Omega$$

$$V_{AB} = -220(0.0374) - 330(-0.0125)$$

$$V_{AB} = -8.228 + 4.125 = -4.103V$$

Nidhesh Goma

C5-2 16014224025




Academic Year: 2024-25



Norton's Theorem:

I_{sc} / I_N

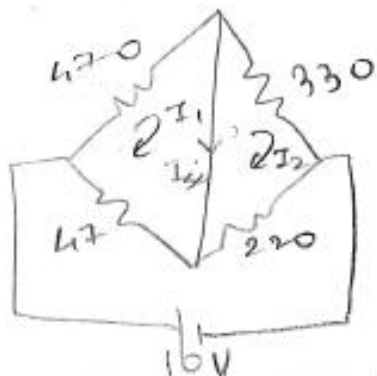

$$-470 I_1 - 47(I_1 - I_3) = 0 \quad \text{--- (i)}$$

$$-330 I_2 - 220(I_2 - I_3) = 0 \quad \text{--- (ii)}$$

$$10 - 47(I_1 - I_3) - 220(I_2 - I_3) = 0 \quad \text{--- (iii)}$$


Nidhesh Gama
CS-2 16014224025
Nidhesh

Observation Table:

	V_{TH} (V)	R_{TH} / R_N (Ω)	I_N (mA)	I_L (mA)
Theoretical value	-4.103V	232.60 Ω	-17.6	-12.3
Practical value	-4.10V	231.2 Ω	-17.4	-12.1

Draw Thevenin's Equivalent circuit

$$R_{th} = 232.60$$

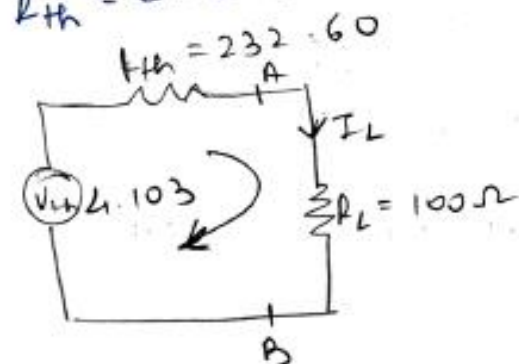


$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{-4.103}{332.60}$$

$$I_L = -0.0123 \text{ A}$$

$$I_L = -12.3 \text{ mA}$$

Draw Norton's Equivalent circuit

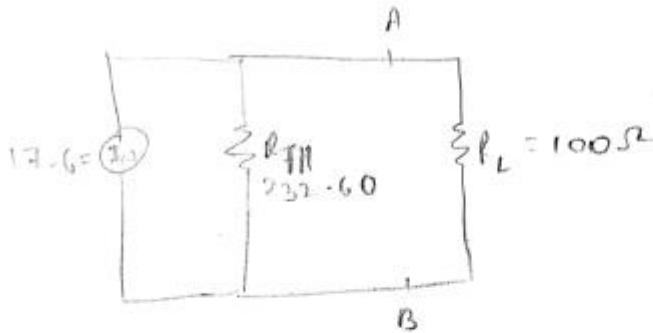

Nidhesh Goma
CS-2 16014224025
Nidhesh

Conclusion:

We understood to analyze resistive networks using DC source. we ~~cannot~~ learned how to deal with resistances on bread board.

Signature of faculty in-charge with Date: