

<b>Course Name:</b>	Elements of Electrical and Electronics Engineering	<b>Semester:</b>	I/II
<b>Date of Performance:</b>	11 /9/ 2024	<b>Batch No:</b>	C5-2
<b>Student Name:</b>	Nidhesh Gomai	<b>Roll No:</b>	16014224025
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	/ 20

## Experiment No: 4

### Title: Maximum Power Transfer Theorem

#### Aim and Objective of the Experiment:


- To observe maximum power transfer across load resistor in a D.C circuit.

#### COs to be achieved:

**CO1:** Analyze resistive networks excited by DC sources using various network theorems.
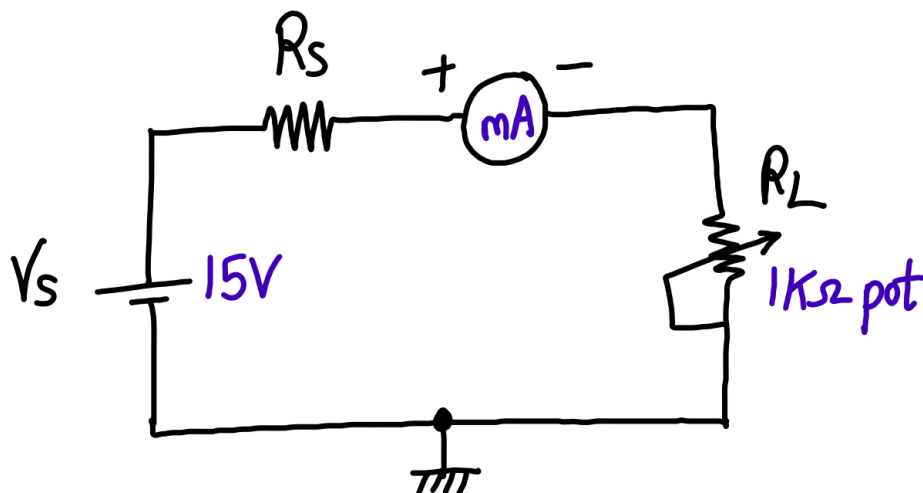
#### Circuit Diagram:

$V_s = 15\text{ V}$  and  $R_s = \underline{560\ \Omega}$




### Stepwise-Procedure:

1. Set D.C. supply voltage  $V_S = 15\text{ V}$
2. Vary  $R_L$  in the range  $100\ \Omega$  -  $1\text{ K}\Omega$  in steps of  $100\ \Omega$
3. Note down  $I_L$  and  $V_L$  for each value of  $R_L$ . Where  $I_L$  and  $V_L$  are current through  $R_L$  and voltage across  $R_L$  respectively.
4. Prepare observation table showing readings of  $R_L$  Vs power  $P = I_L \cdot V_L$
5. Plot graph of  $P$  Vs  $R_L$
6. Locate the point of maximum value of power  $P$  and note down corresponding value of  $R_L$ .  
Verify the results theoretically

### Observation Table:

Sr. No.	$R_L\ \Omega$	Circuit Current ( $I_L$ ) in mA		Voltage ( $V_L$ ) in Volts	Power absorbed by load ( $P_L$ ) in $P_L = I_L^2 \cdot R_L$	
		Theoretical	Practical		Theoretical	Practical
1.	100	22.7	22	2.1	0.0515	0.0441
2.	200	19.7	18	4	0.07761	0.08
3.	300	17.7	16	5.16	0.0908	0.088
4.	400	15.6	14	6.32	0.0973	0.099
5.	500	14.5 13.3	14 12	7.09 7.52	0.1001 0.1004	0.1005 0.1009
6.	600	12.93	12	7.78	0.0849	0.1008
7.	700	11.90	10	8.26	0.0991	0.097
8.	800	11.02	10	8.78	0.9715	0.096
9.	900	10.27	10	9.20	0.0953	0.094
10.	1 K	9.61	9	9.65	0.0924	0.093

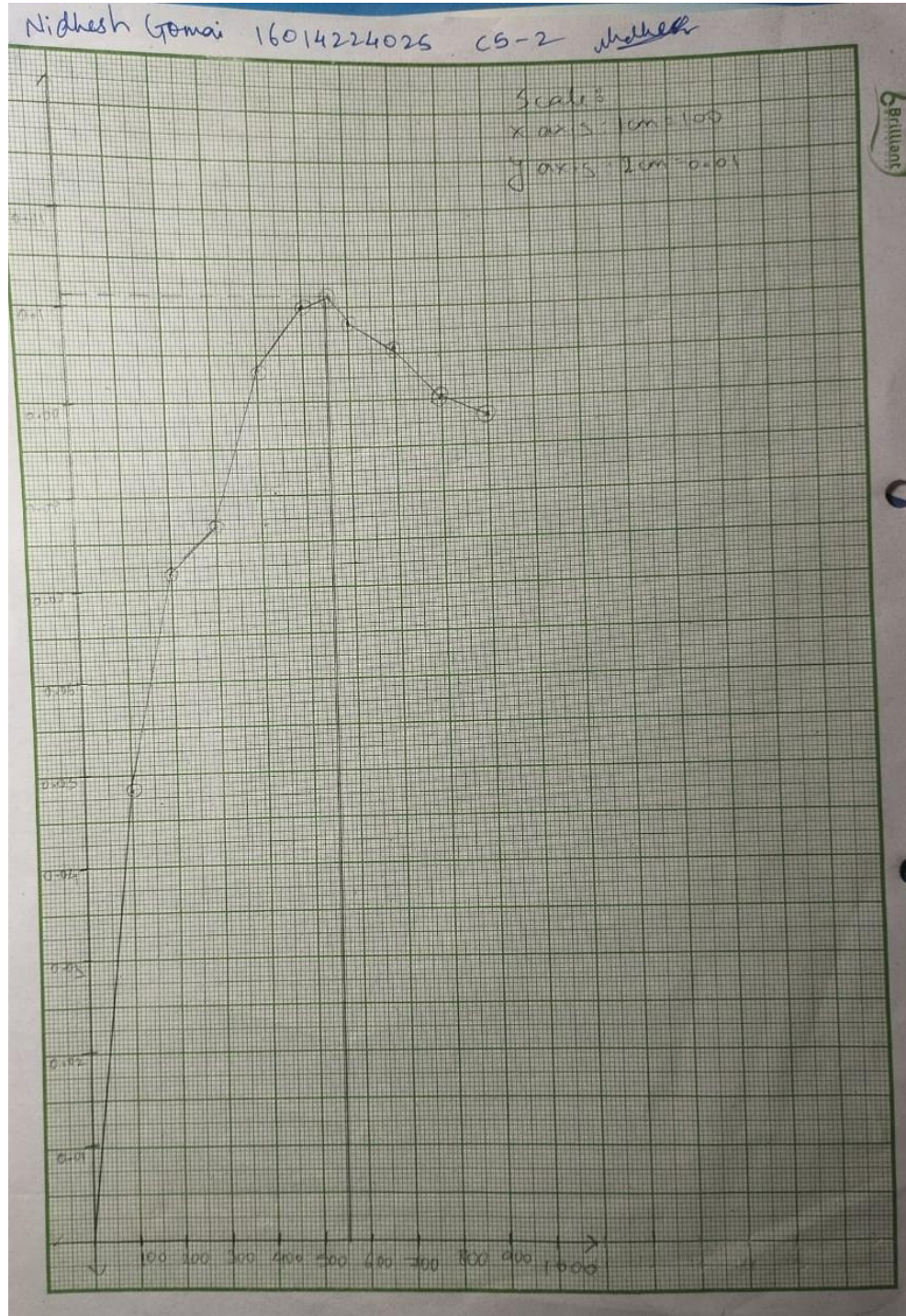**Graph:** Draw a graph showing effect of variation in  $R_L$  on  $P_L$  using observation table. Take  $R_L$  on X-axis and  $P_L$  on Y-axis. (Use a graph paper)



**Conclusion-**



1. Explore one practical application where Maximum Power Transfer Theorem is used.
2. Draw a block diagram or circuit diagram of this application.
3. Explain in brief.

**OR**

**Answer the following:**

4. Do you apply Thevenin's Theorem to calculate Maximum Power across load resistor in a D.C. circuit?
5. Take a sample problem. Draw a block diagram or circuit diagram of this sample problem.
6. Explain the solution in brief.

**Signature of faculty in-charge with Date:**